
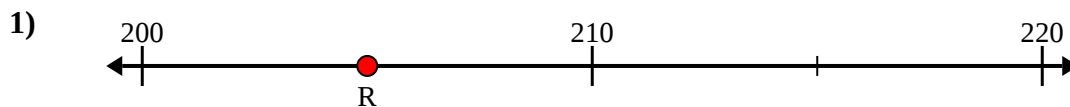


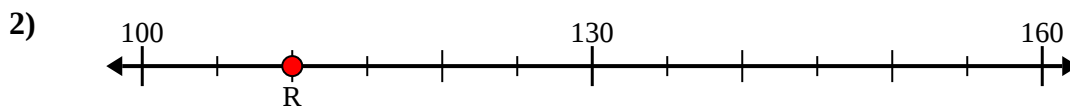


Find the value of R.

Answers


1. _____




2. _____

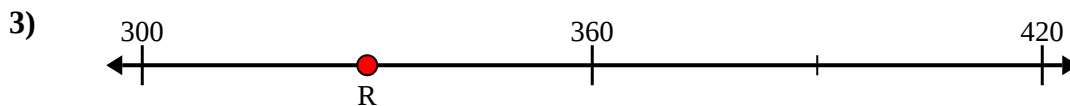


3. _____

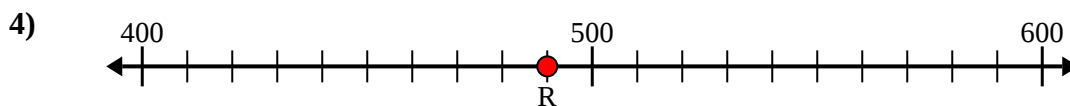


4. _____

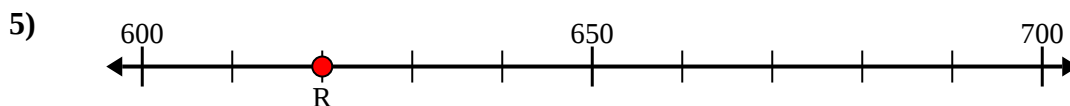


5. _____

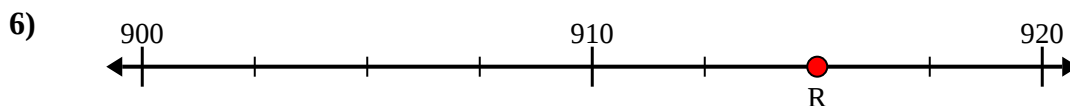


6. _____

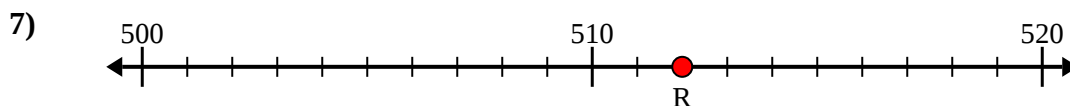


7. _____

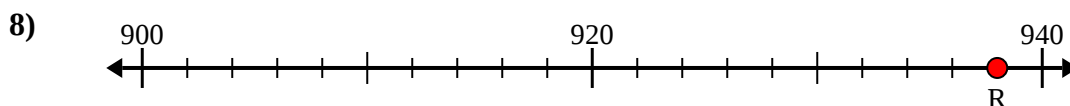

8. _____

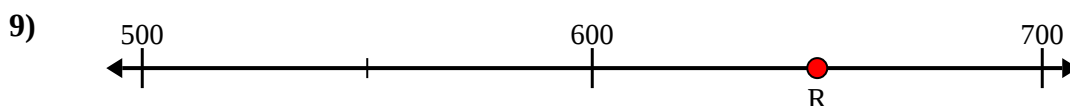











9. _____

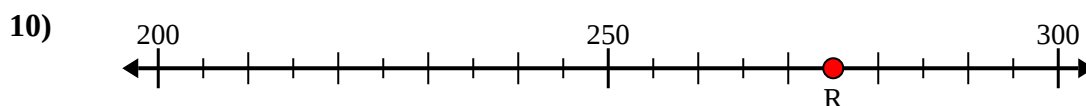

10. _____




Find the value of R.

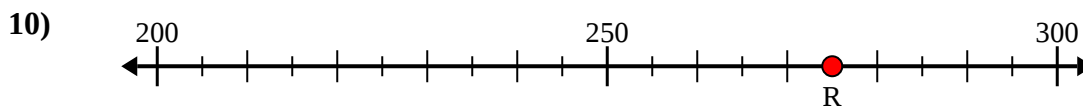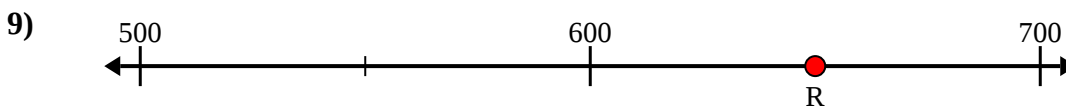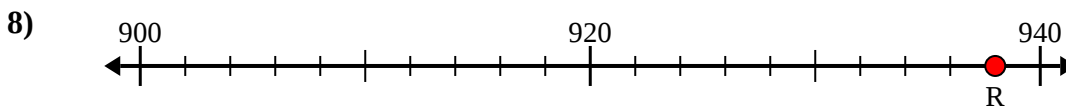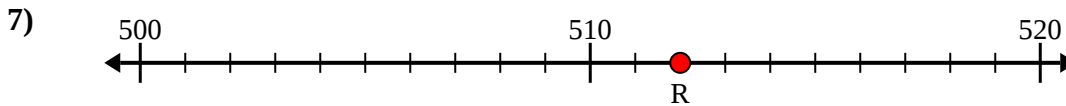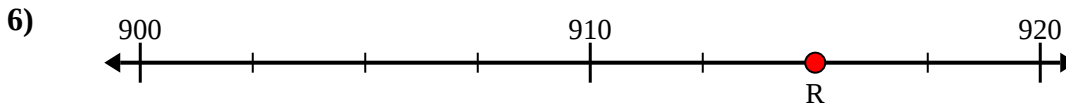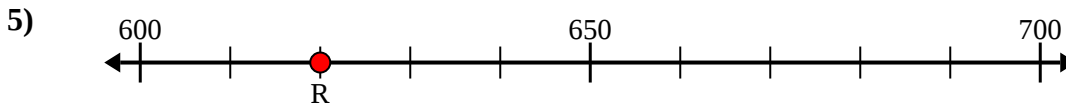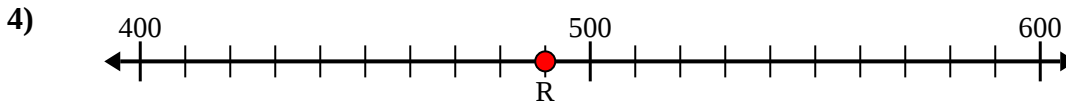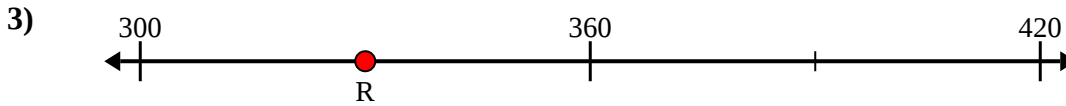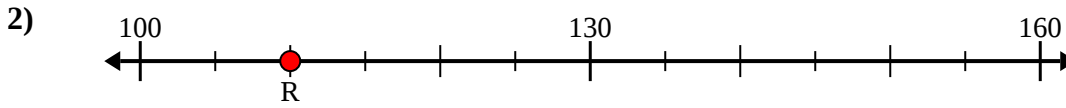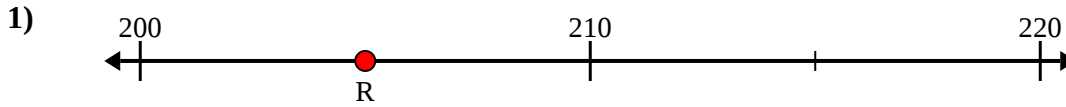**Answers**


1. **205**
2. **110**
3. **330**
4. **490**
5. **620**
6. **915**
7. **512**
8. **938**
9. **650**
10. **275**




Find the value of R.

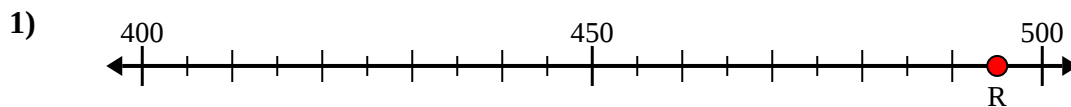Answers


1. _____

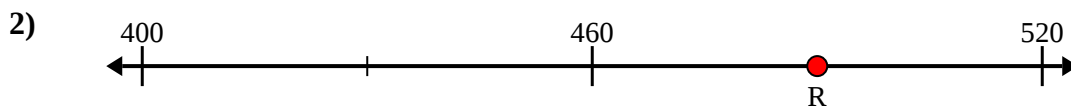


2. _____

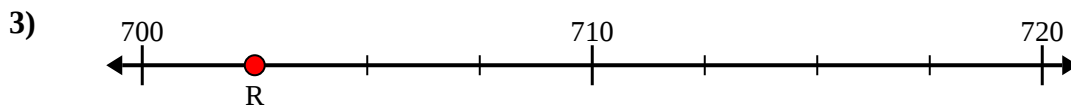


3. _____

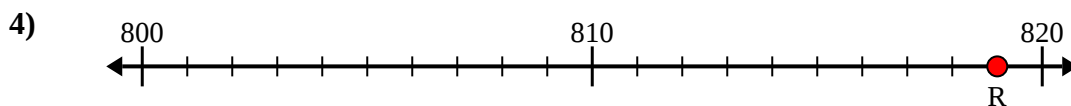


4. _____

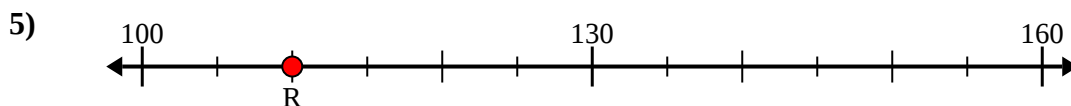


5. _____

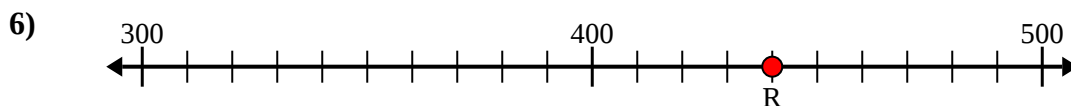


6. _____

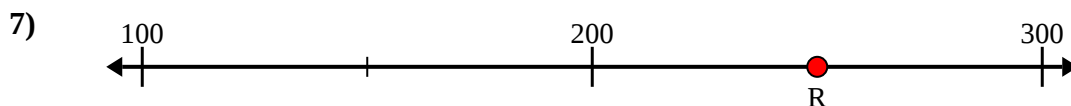


7. _____

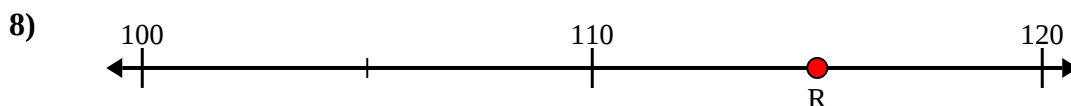

8. _____

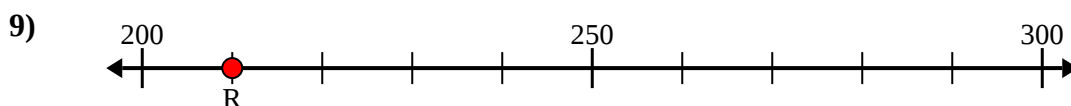











9. _____

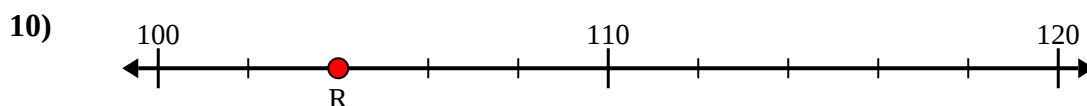

10. _____




Find the value of R.

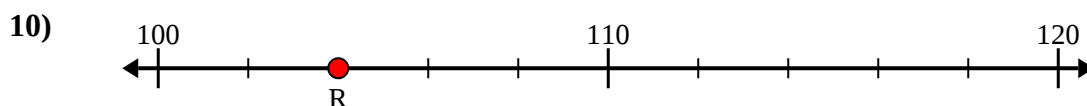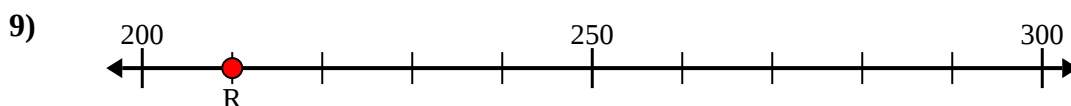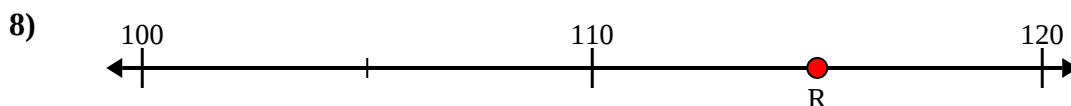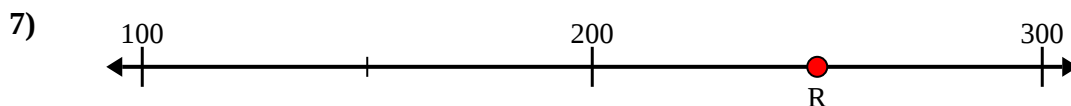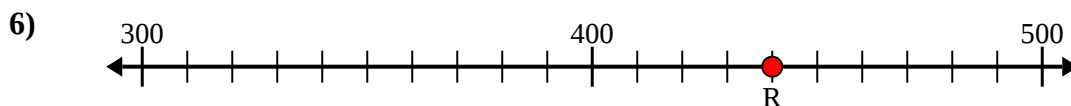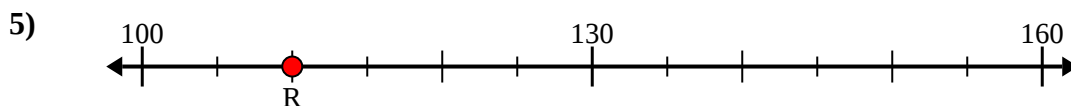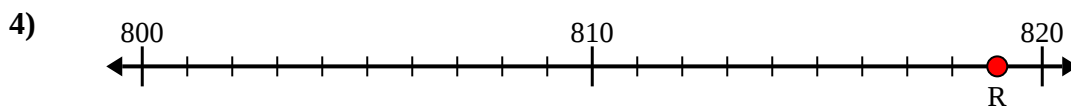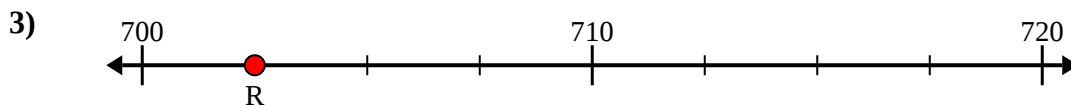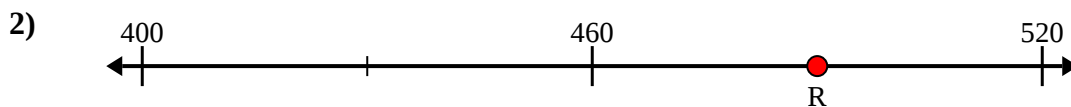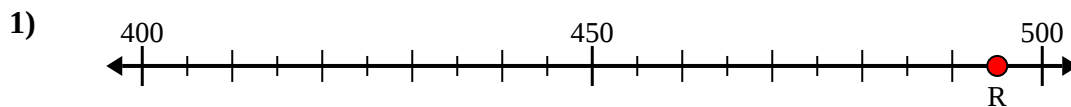
**Answers**1. **495**2. **490**3. **702.5**4. **819**5. **110**6. **440**7. **250**8. **115**9. **210**10. **104**




Find the value of R.

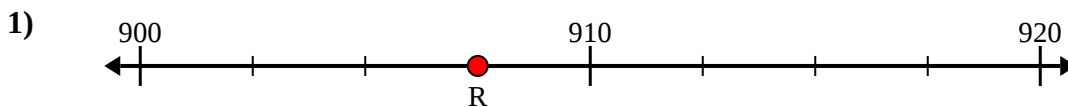Answers


1. _____

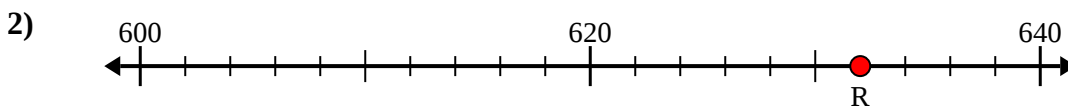


2. _____

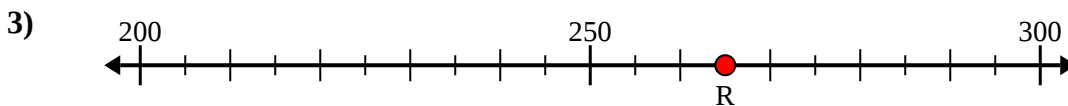


3. _____

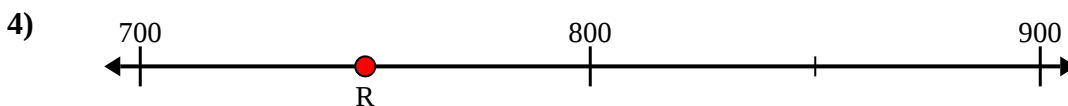


4. _____

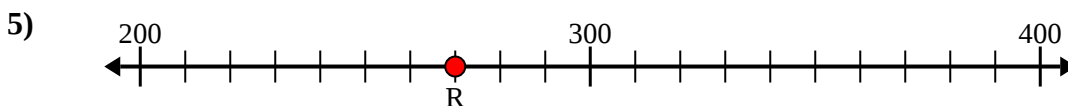


5. _____

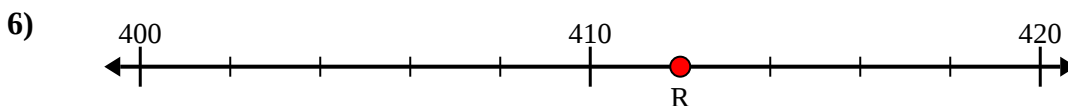


6. _____

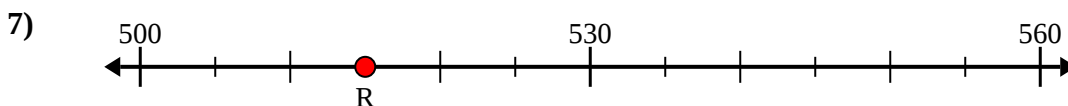


7. _____

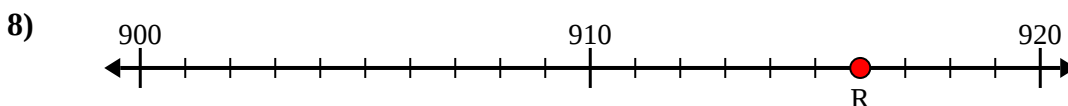

8. _____

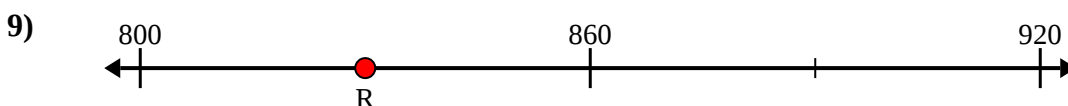











9. _____

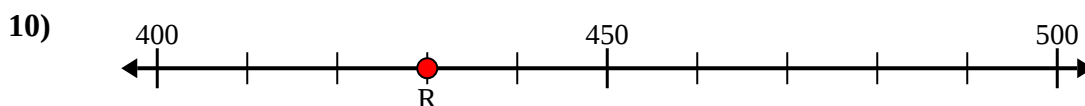

10. _____




Find the value of R.

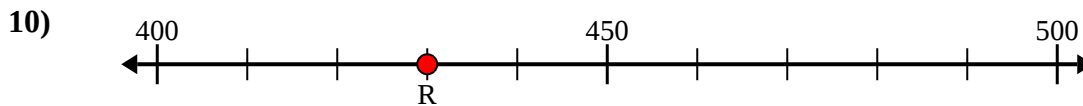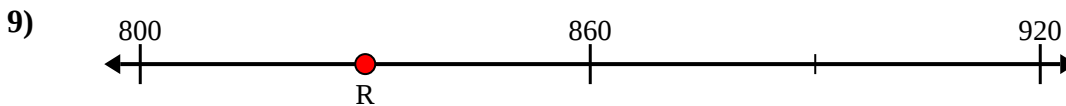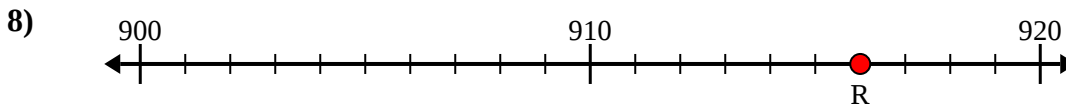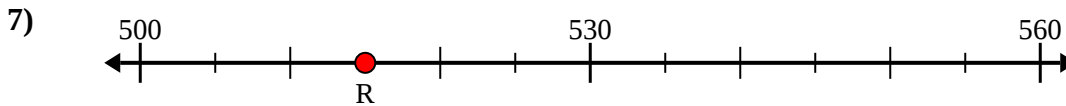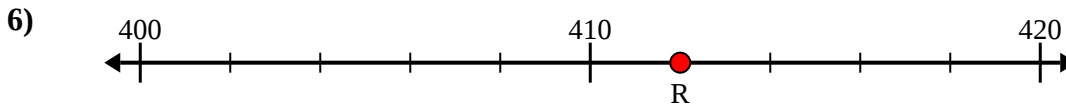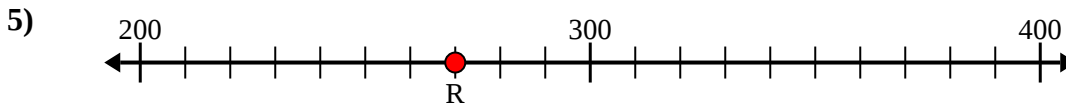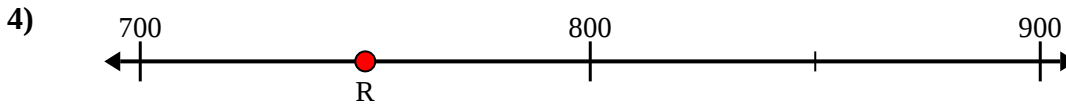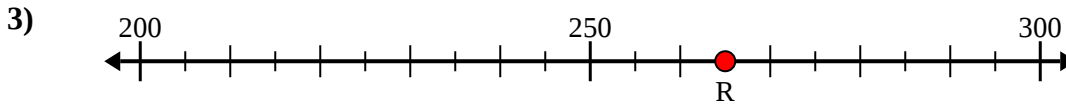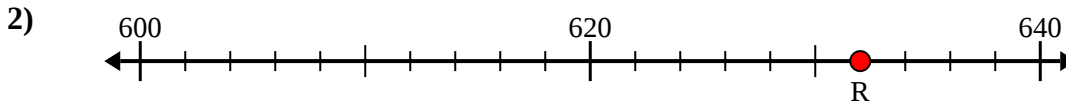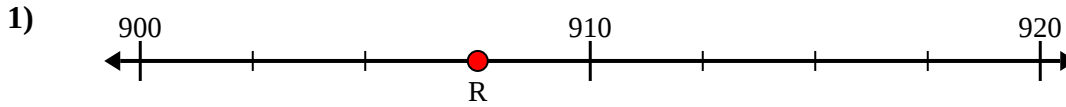
**Answers**1. **907.5**2. **632**3. **265**4. **750**5. **270**6. **412**7. **515**8. **916**9. **830**10. **430**




Find the value of R.

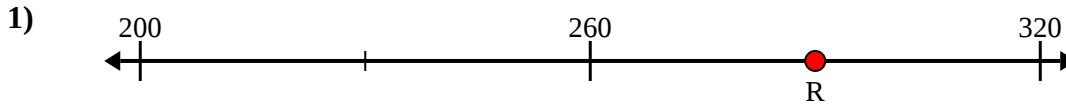Answers


1. _____

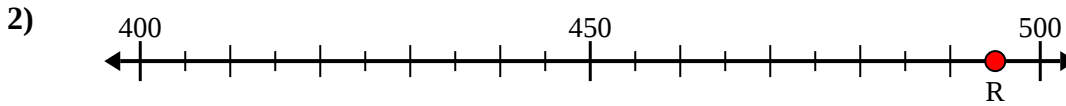


2. _____

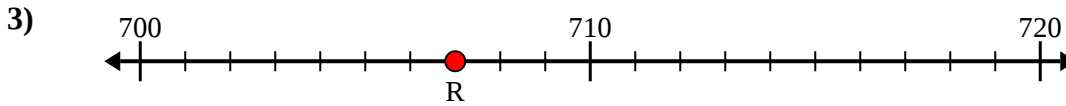


3. _____

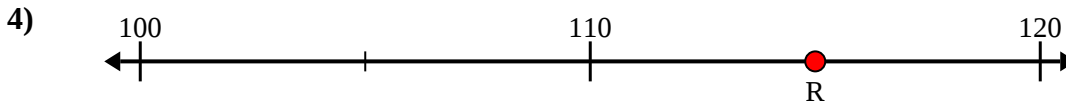


4. _____

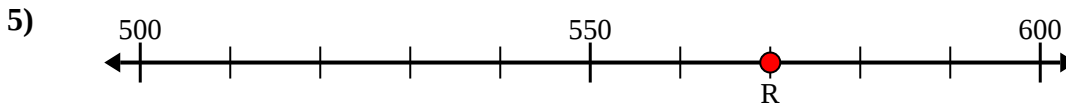


5. _____

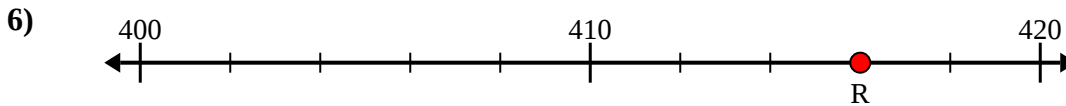


6. _____

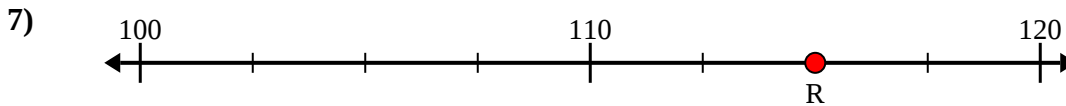


7. _____

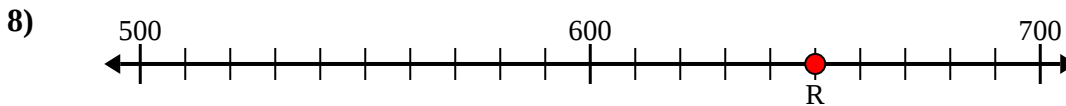

8. _____

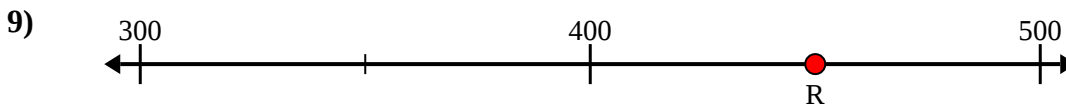











9. _____

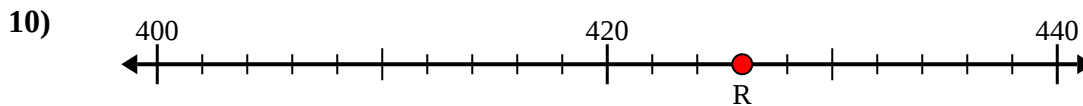

10. _____




Find the value of R.

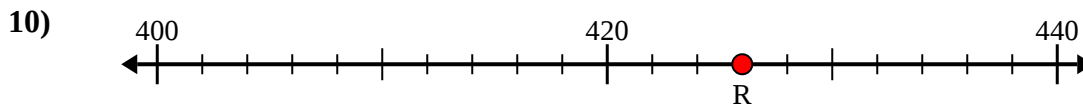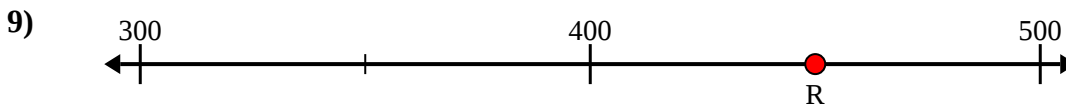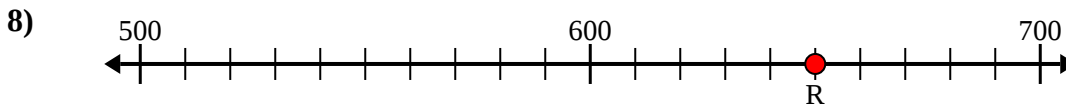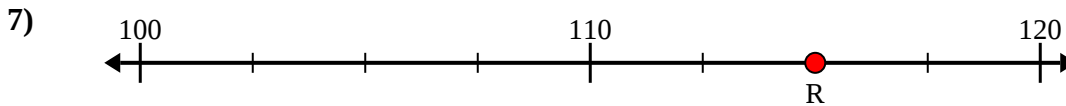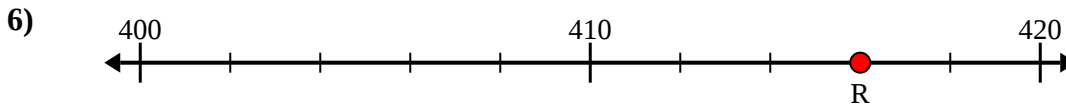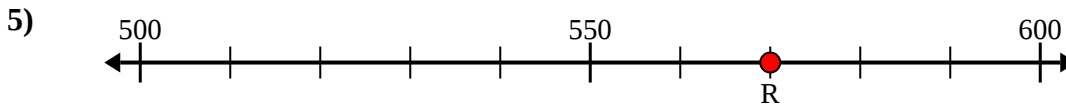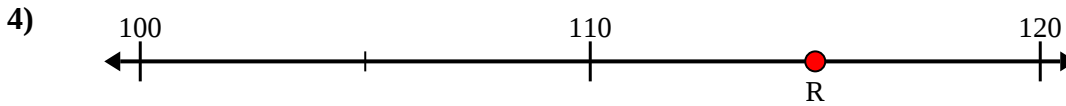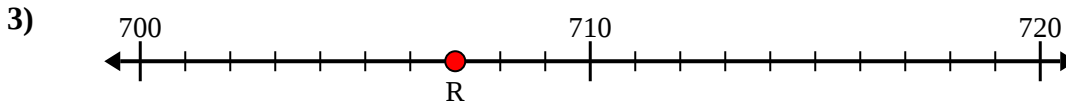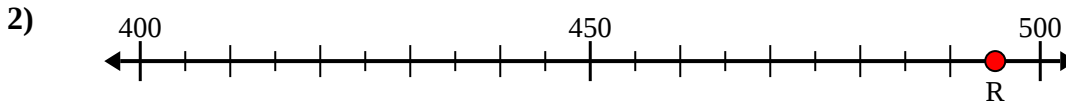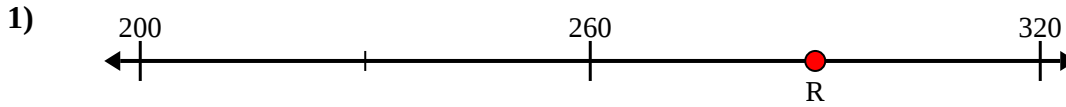
**Answers**1. **290**2. **495**3. **707**4. **115**5. **570**6. **416**7. **115**8. **650**9. **450**10. **426**




Find the value of R.

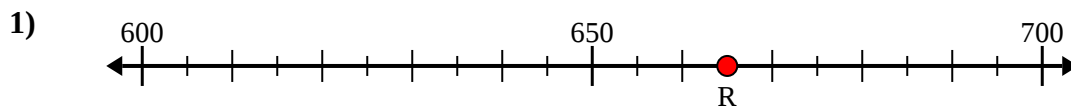Answers


1. _____

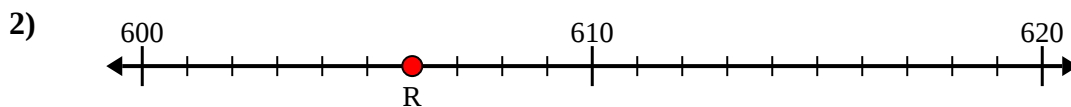


2. _____

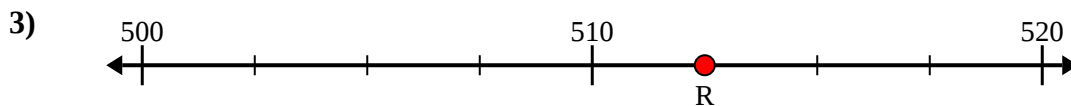


3. _____

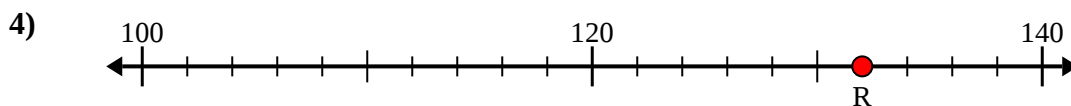


4. _____

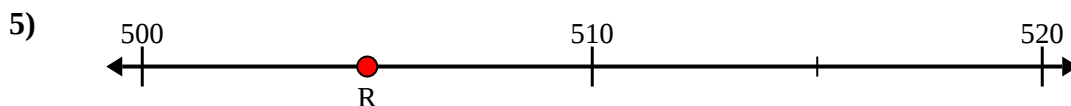


5. _____

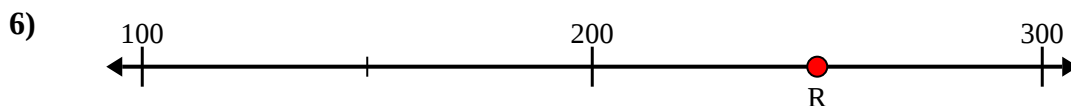


6. _____

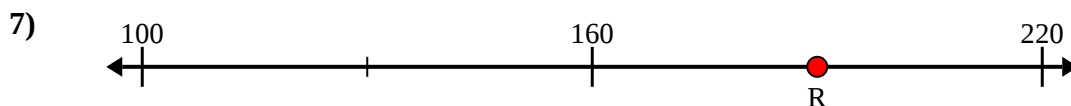


7. _____

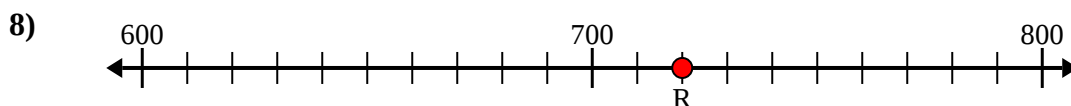

8. _____

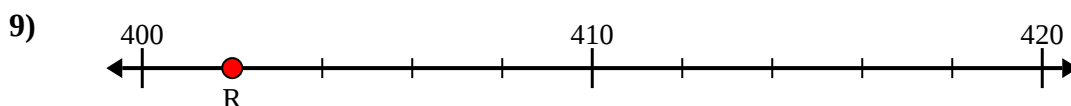











9. _____

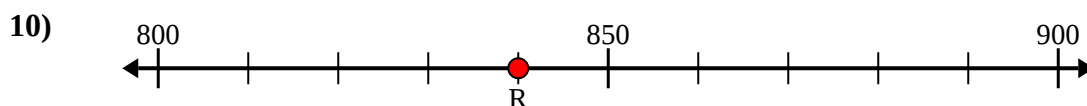

10. _____




Find the value of R.

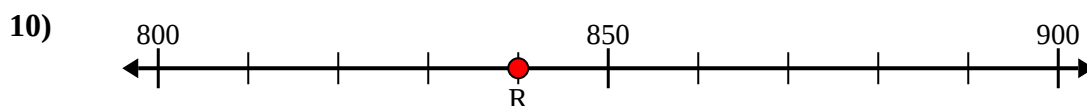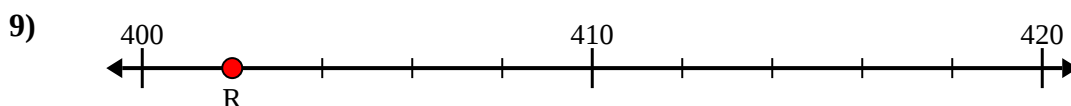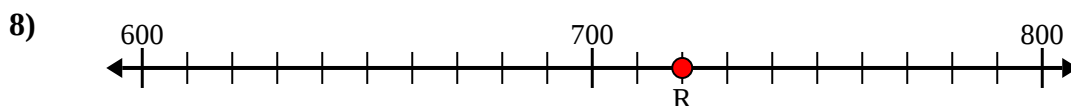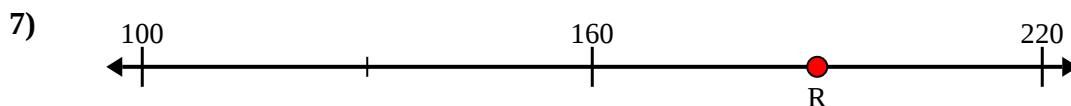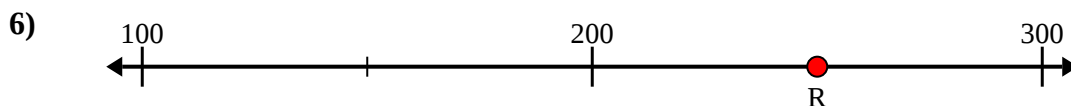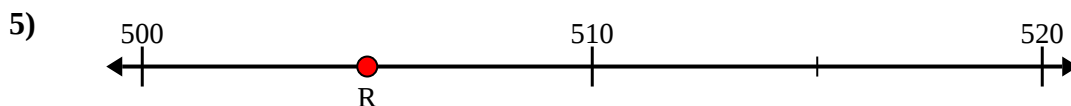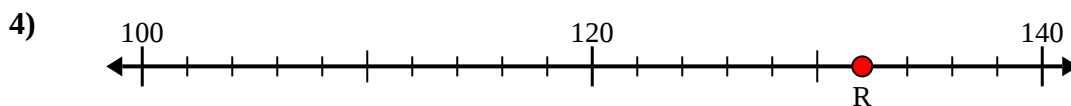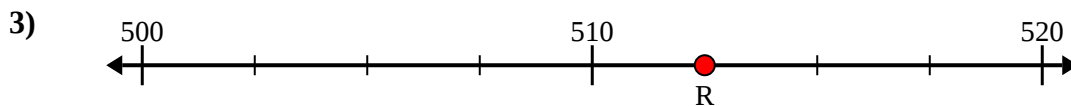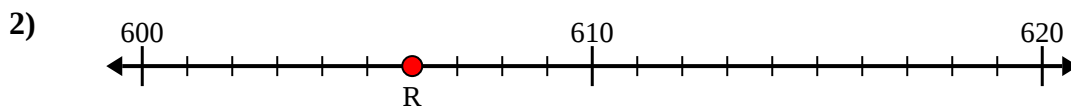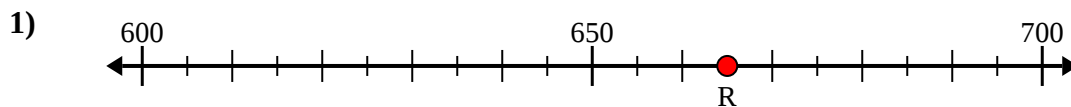
Answers1. **665**2. **606**3. **512.5**4. **132**5. **505**6. **250**7. **190**8. **720**9. **402**10. **840**




Find the value of R.

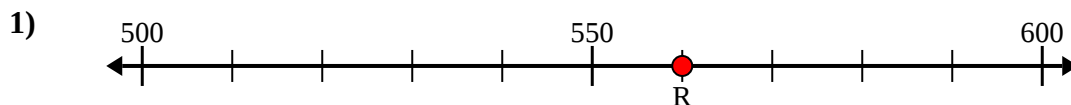Answers


1. _____

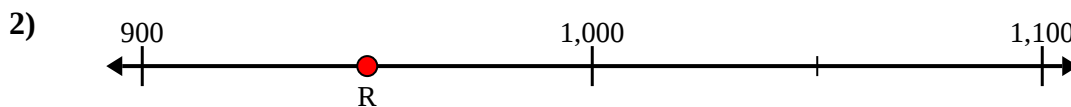


2. _____

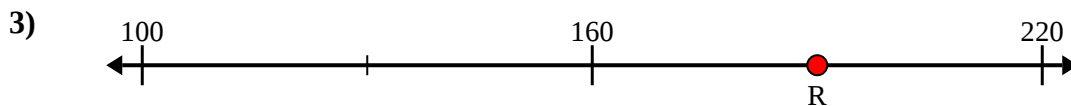


3. _____

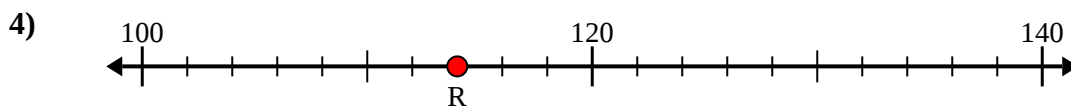


4. _____

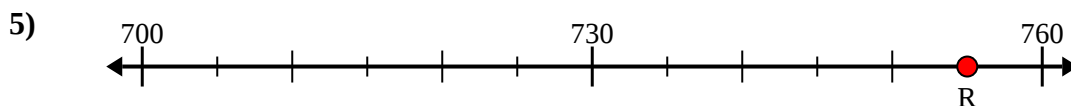


5. _____

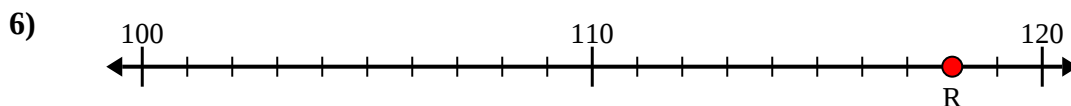


6. _____

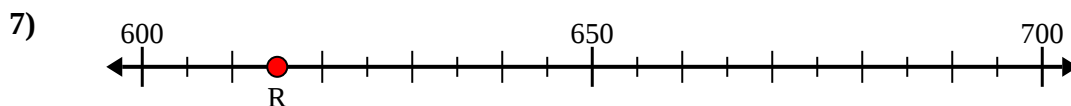


7. _____

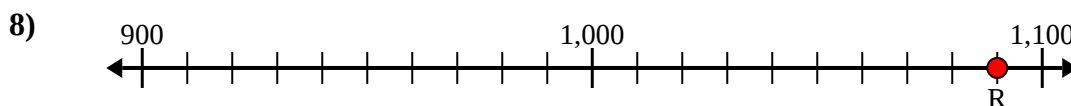

8. _____

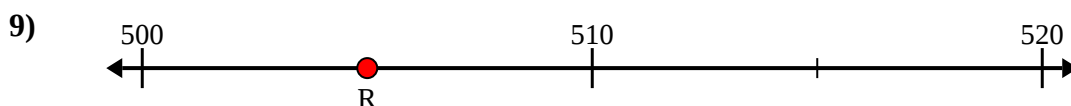











9. _____

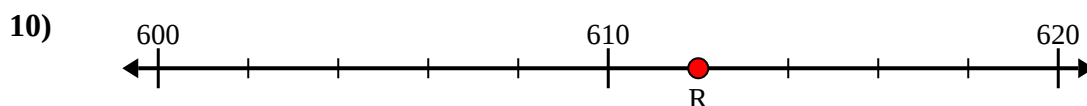

10. _____




Find the value of R.

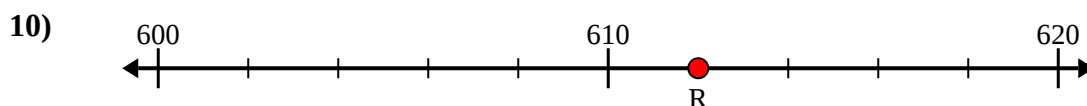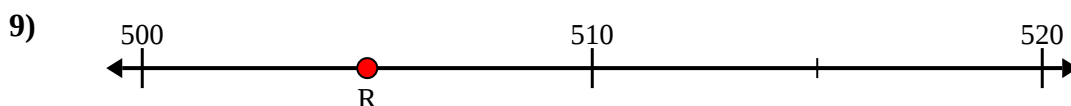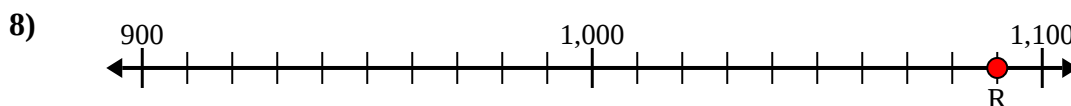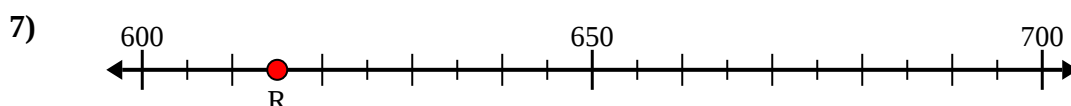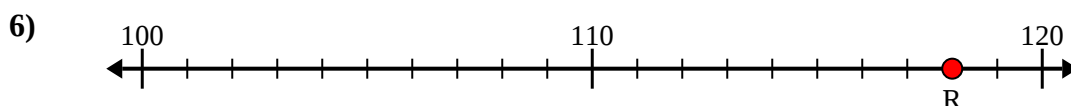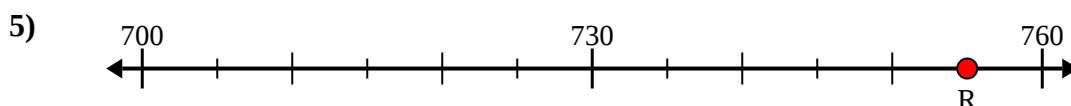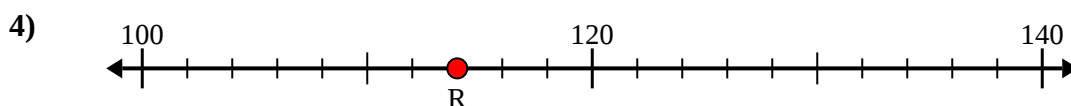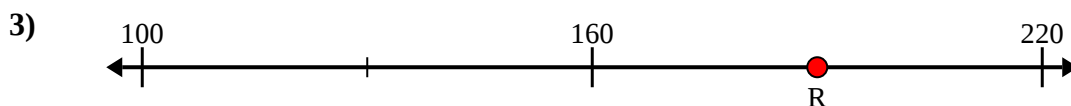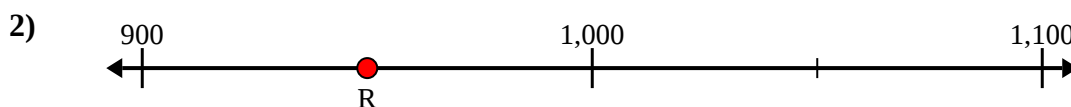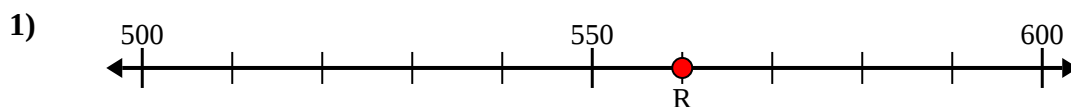
**Answers**1. **560**2. **950**3. **190**4. **114**5. **755**6. **118**7. **615**8. **1,090**9. **505**10. **612**




Find the value of R.

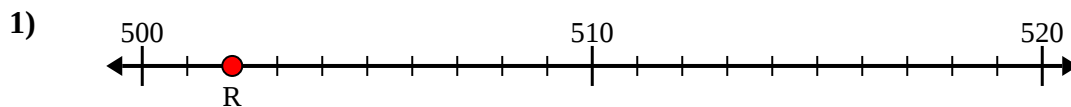Answers


1. _____

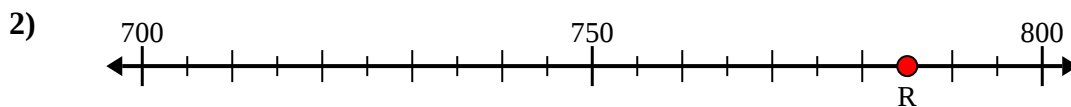


2. _____

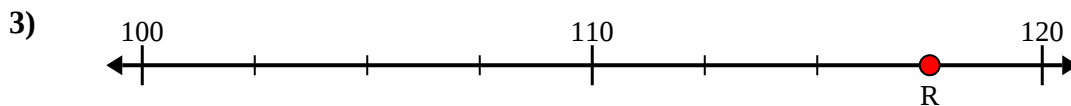


3. _____

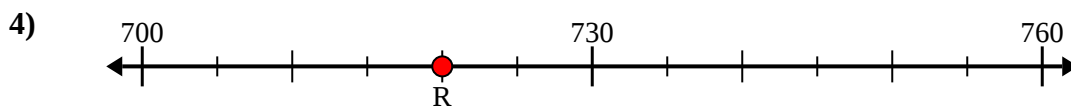


4. _____

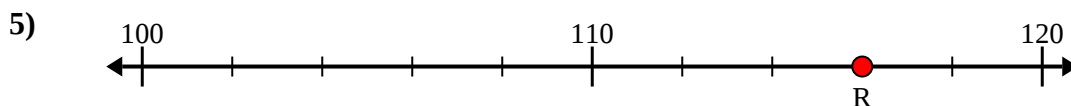


5. _____

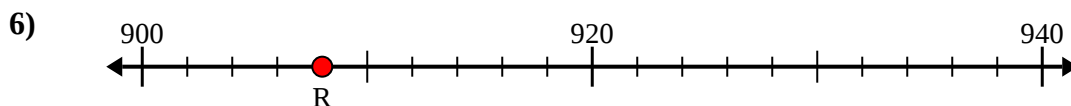


6. _____

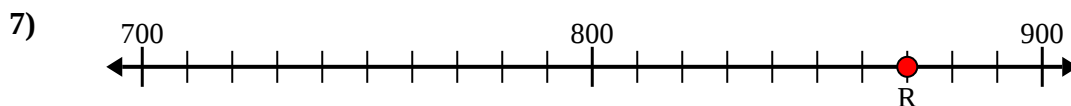


7. _____

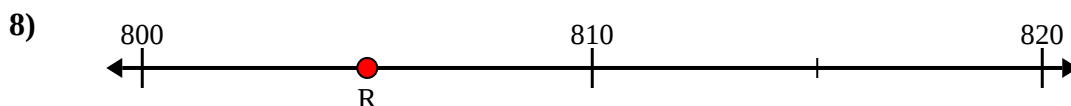

8. _____

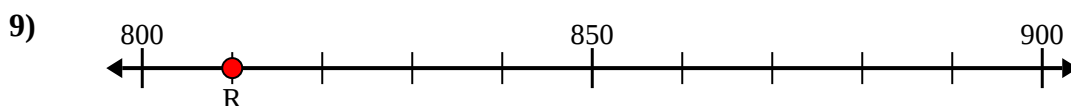











9. _____

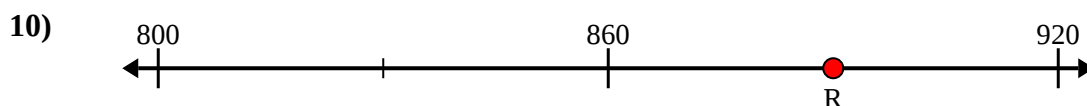

10. _____




Find the value of R.

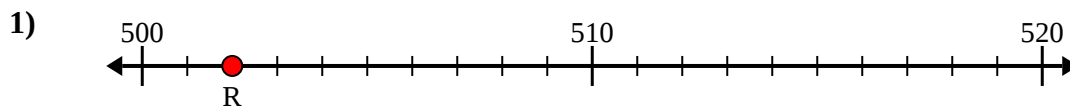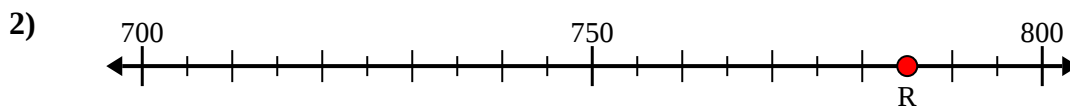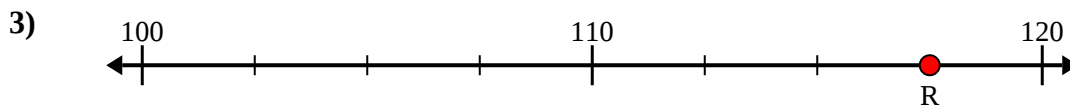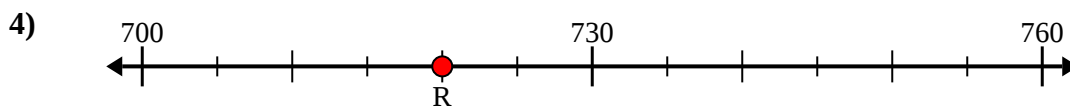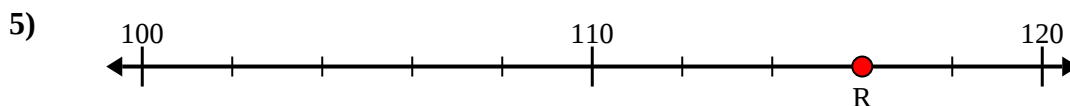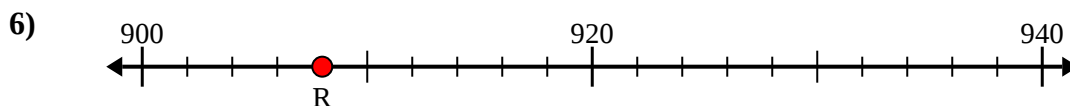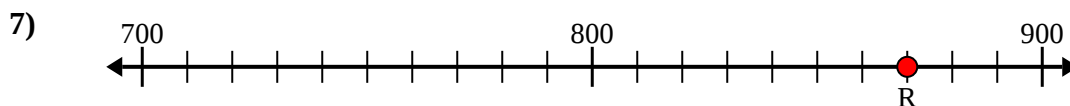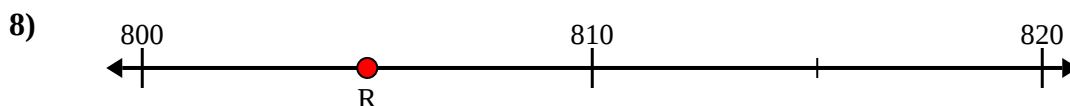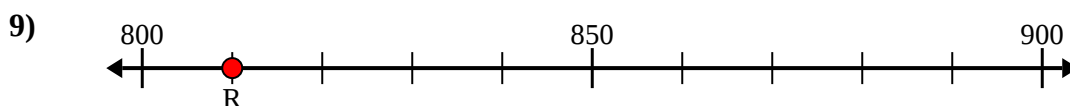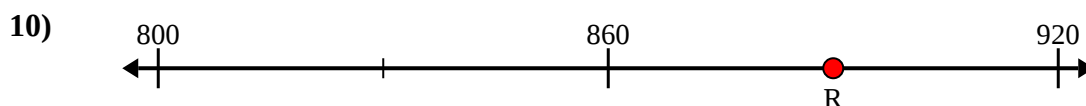
Answers1. **502**2. **785**3. **117.5**4. **720**5. **116**6. **908**7. **870**8. **805**9. **810**10. **890**




Find the value of R.

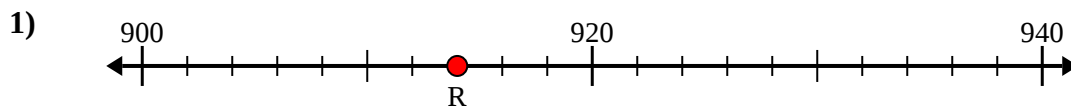Answers


1. _____

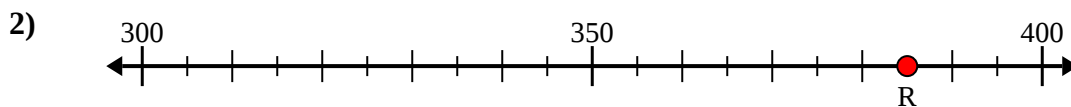


2. _____

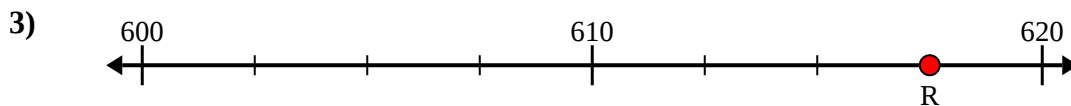


3. _____

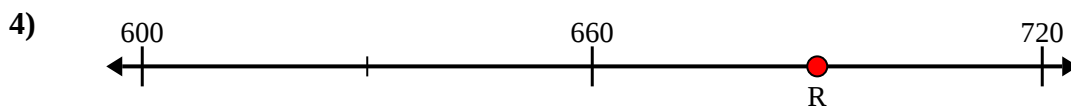


4. _____

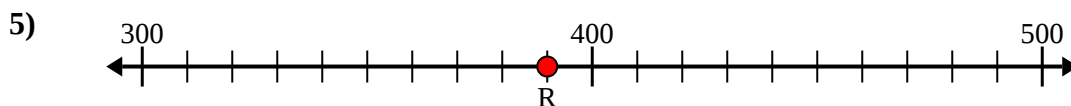


5. _____

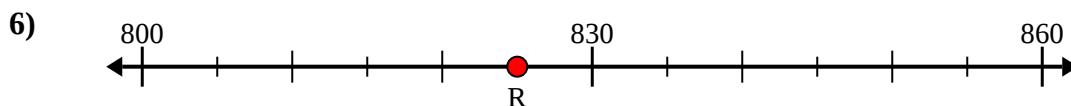


6. _____

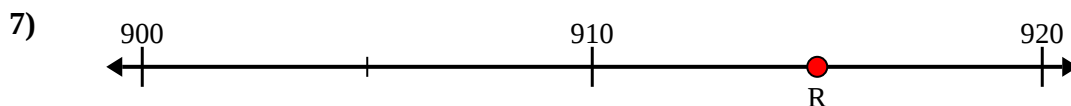


7. _____

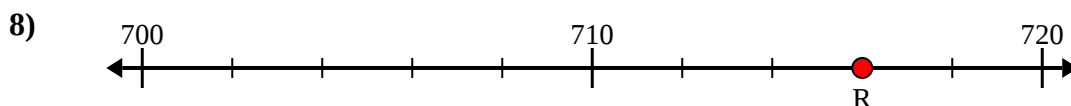

8. _____

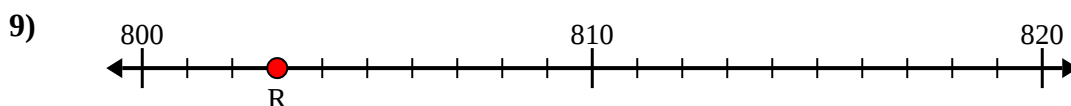











9. _____

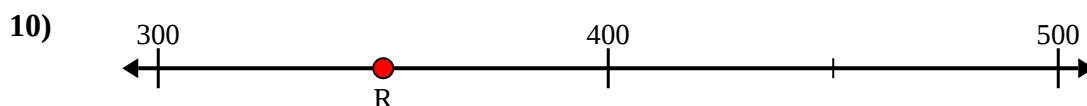

10. _____




Find the value of R.

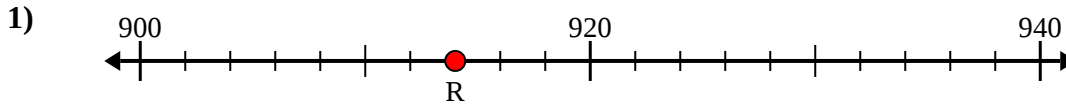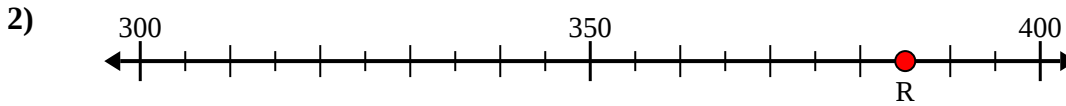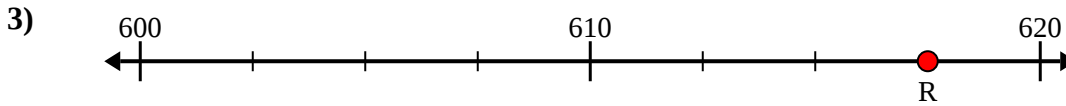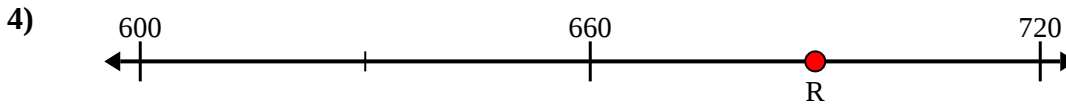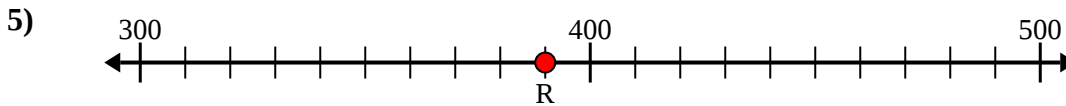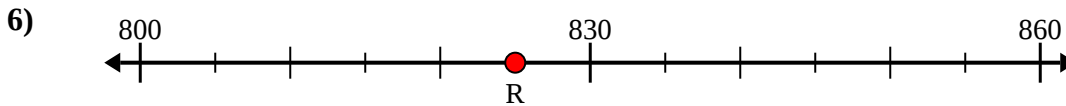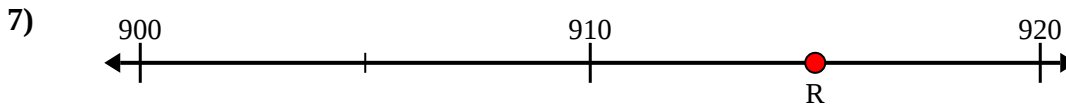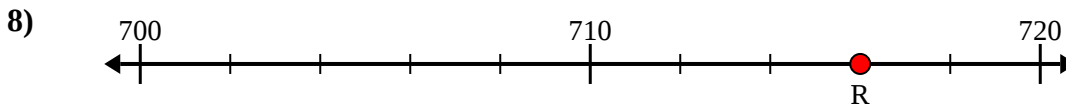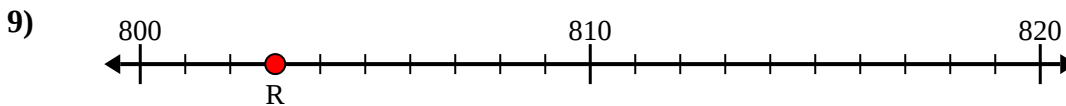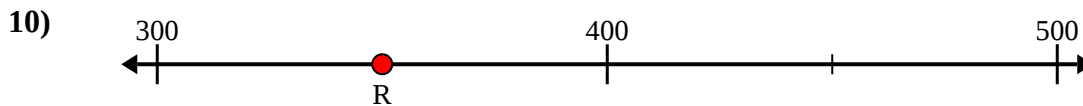
Answers1. **914**2. **385**3. **617.5**4. **690**5. **390**6. **825**7. **915**8. **716**9. **803**10. **350**




Find the value of R.

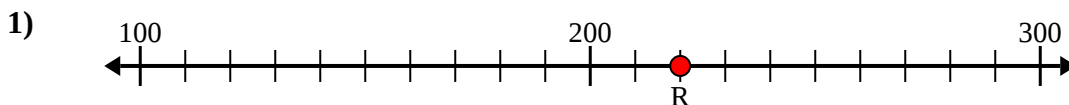Answers


1. _____

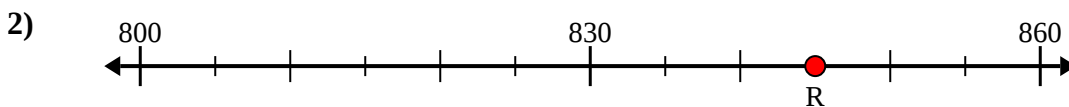


2. _____

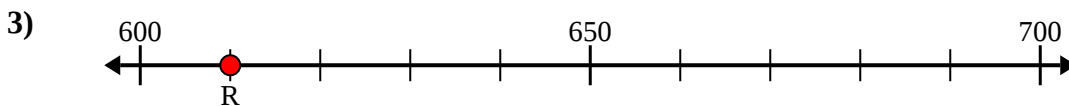


3. _____

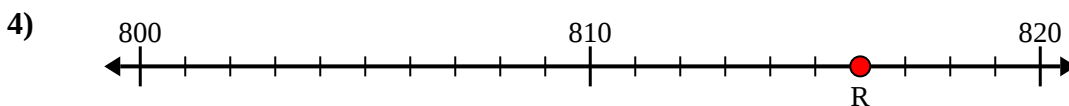


4. _____

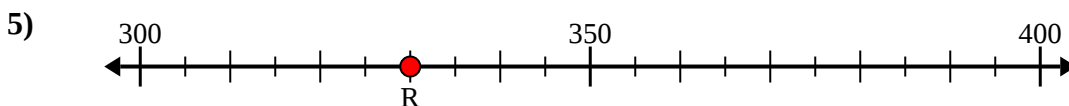


5. _____

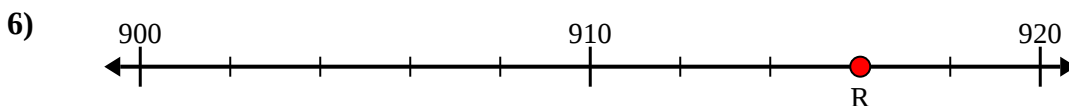


6. _____

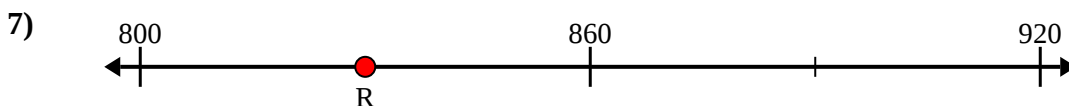


7. _____

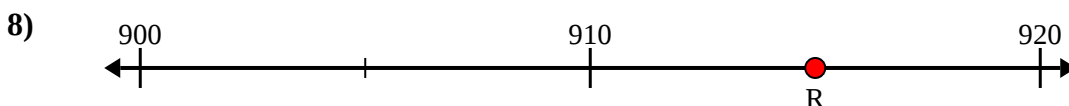

8. _____

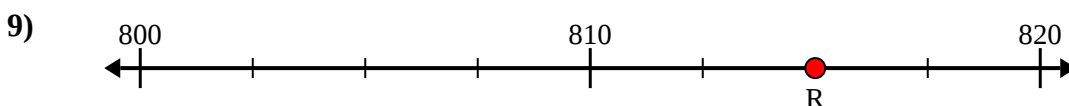











9. _____

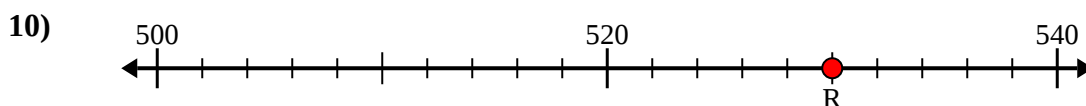

10. _____




Find the value of R.

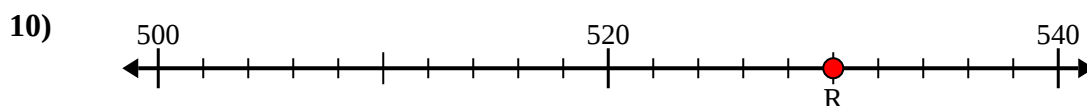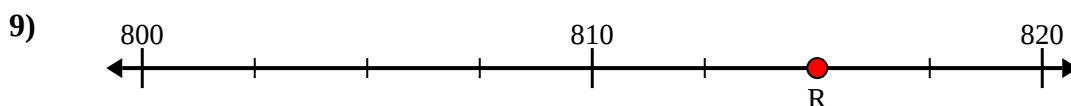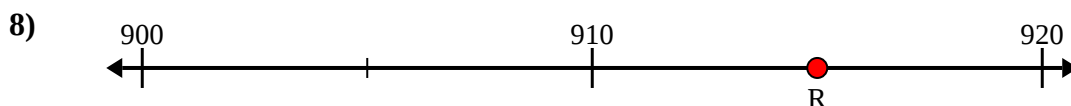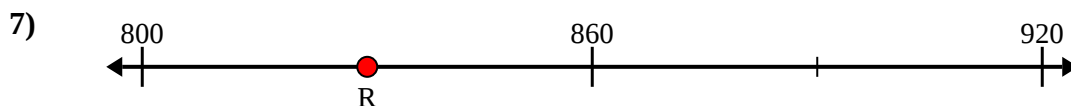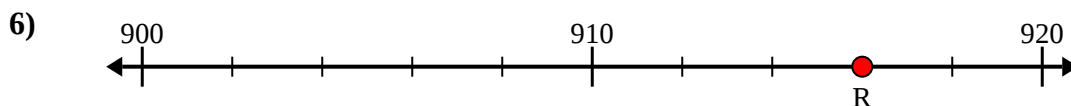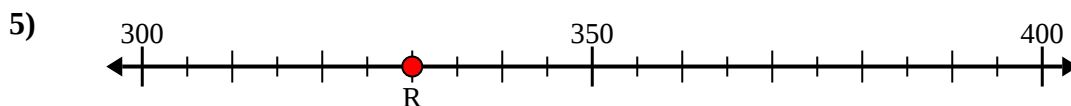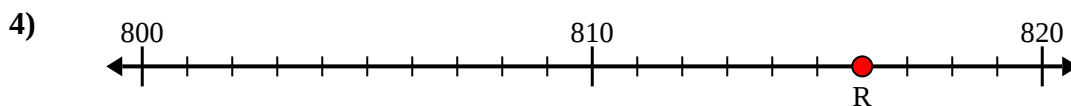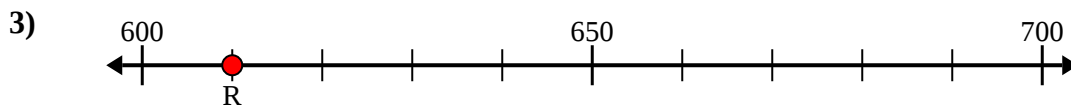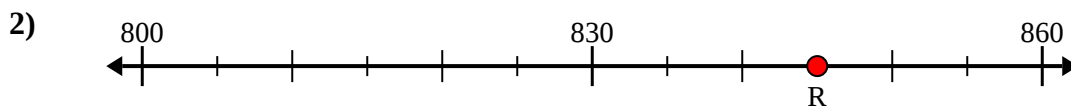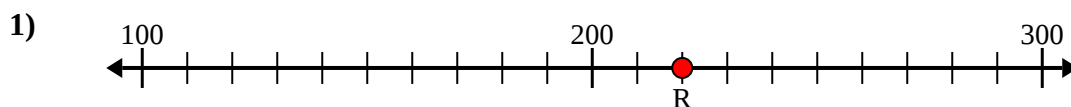
Answers1. **220**2. **845**3. **610**4. **816**5. **330**6. **916**7. **830**8. **915**9. **815**10. **530**




Find the value of R.

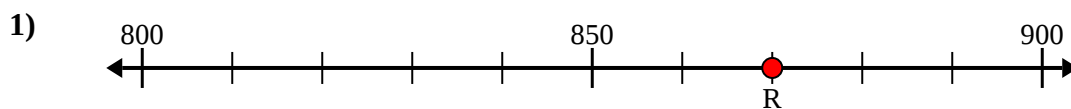Answers


1. _____

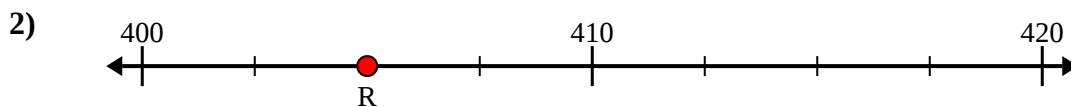


2. _____

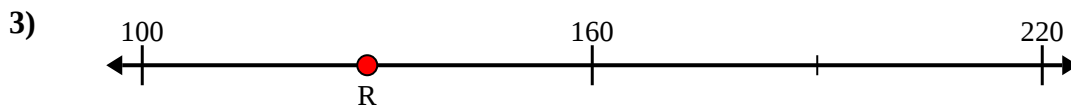


3. _____

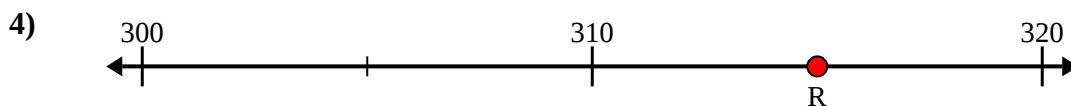


4. _____

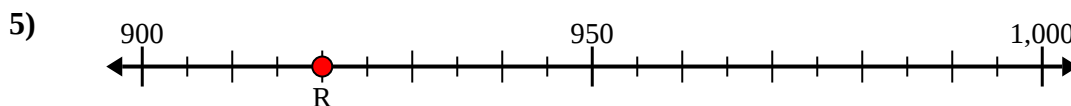


5. _____

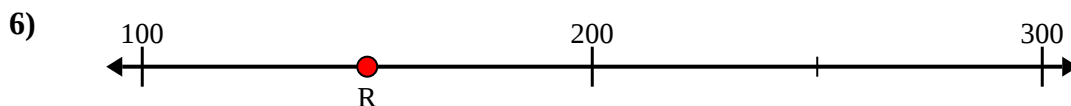


6. _____

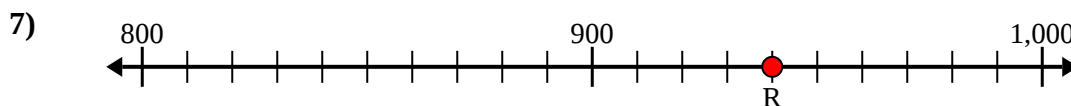


7. _____

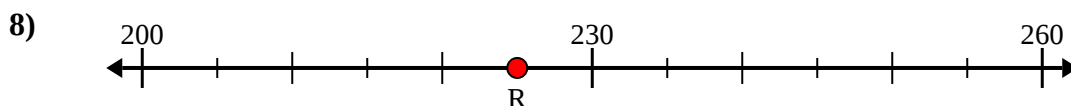

8. _____

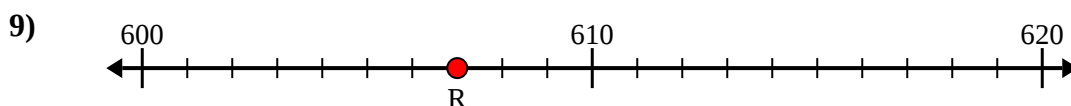











9. _____

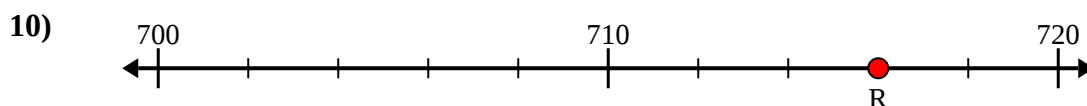

10. _____



Find the value of R.

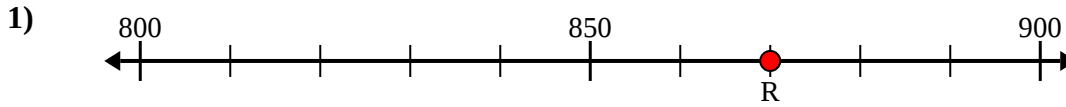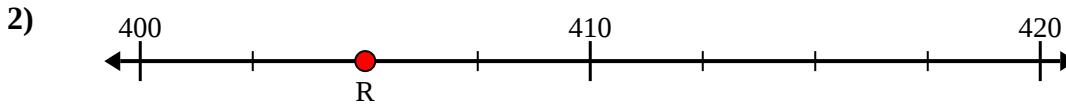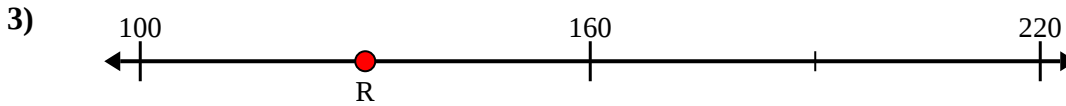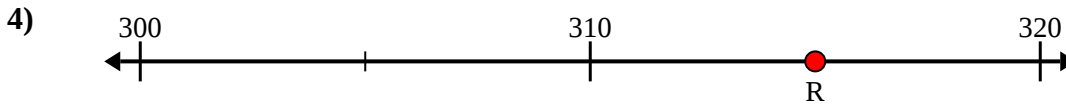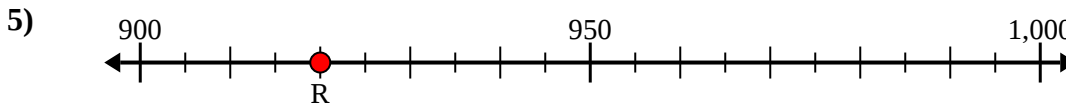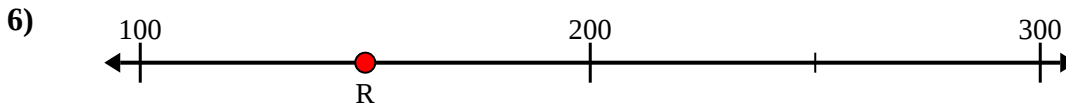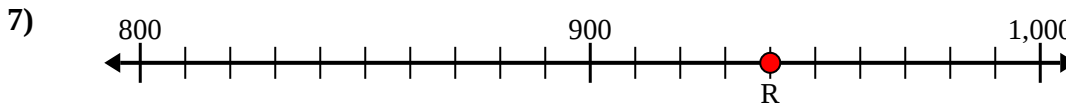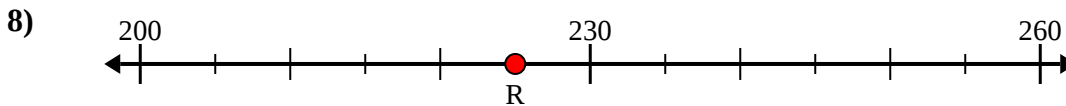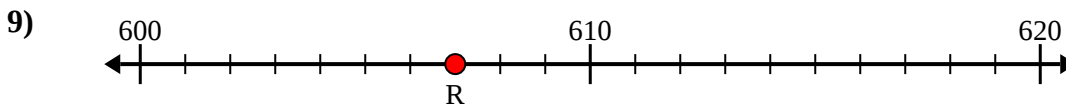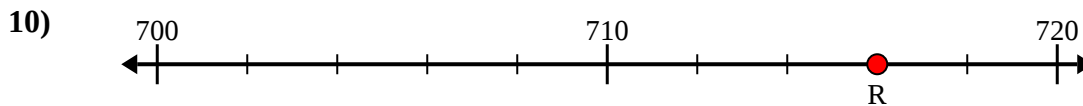Answers1. **870**2. **405**3. **130**4. **315**5. **920**6. **150**7. **940**8. **225**9. **607**10. **716**